

6	<p><b>A is the correct answer</b></p> <p>B is not the correct answer as both the ammeter and voltmeter readings decrease.</p> <p>C is not the correct answer as the voltmeter reading decreases.</p> <p>D is not the correct answer as the ammeter reading decreases.</p>	(1)
7	<p><b>C is the correct answer</b></p>	(1)