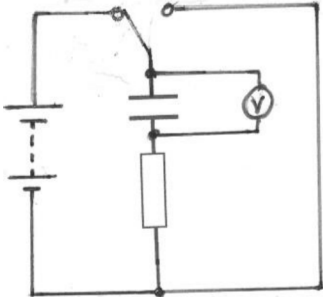
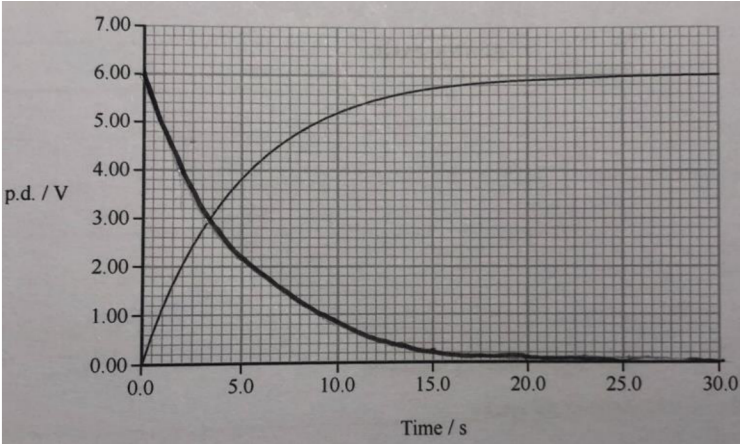


Question number	Answer	Mark
17 (a)	<ul style="list-style-type: none"> Battery in series with capacitor and resistor (1) Voltmeter/datalogger/oscilloscope in parallel with capacitor (1) Appropriate switching mechanism and discharge circuit completed (1) <p><u>Example of diagram:</u></p> 	3
17 (b) (i)	<ul style="list-style-type: none"> Exponential decline (1) Symmetry with charging curve, starts at 6.00 V, curves cross at 3.00 V (1) <p><u>Example of graph</u></p> 	2
17 (b) (ii)	<ul style="list-style-type: none"> Use of $I = I_0 e^{-\frac{t}{RC}}$ with $V = IR$ (1) Apply total p.d. = sum of p.d.s (1) Suitable algebra (1) <p><u>Example of derivation</u></p> $I = I_0 e^{-\frac{t}{RC}}$ $V_R = RI_0 e^{-\frac{t}{RC}}$ $I_0 R = V_0$ $V_R = V_0 e^{-\frac{t}{RC}}$ $V_{\text{cap}} = V_0 - V_R$ $V = V_0 - V_0 e^{-\frac{t}{RC}}$	3

<p>17 (b) (iii)</p>	<ul style="list-style-type: none"> • Use of $V = V_0(1 - 1/e) = 0.63 V_0$ for V at time constant (1) • Read time constant off graph = 4.9 s (allow range 4.5 s to 5.0 s) (1) • Use of time constant = RC (1) • $C = 1.5 \times 10^{-5}$ F, so choose 15 μF capacitor (1) <p>($C = 1.4 \times 10^{-5}$ F to $C = 1.5 \times 10^{-5}$ F when rounded to 2 s.f.)</p> <p>Or</p> <ul style="list-style-type: none"> • Draws tangent to line at $t = 0$ s to intercept p.d. = 6.00 V line (1) • Read time constant off graph = 4.9 s (allow range 4.5 s to 5.0 s) (1) • Use of time constant = RC (1) • $C = 1.5 \times 10^{-5}$ F, so choose 15 μF capacitor (1) <p>($C = 1.4 \times 10^{-5}$ F to $C = 1.5 \times 10^{-5}$ F when rounded to 2 s.f.)</p> <p>Or</p> <ul style="list-style-type: none"> • Record corresponding values of V and t from point (or points) on graph (1) • Use of $V = V_0 - V_0 e^{-\frac{t}{RC}}$ (1) • Convert to correct logarithmic form (1) • $C = 1.5 \times 10^{-5}$ F, so choose 15 μF capacitor (1) <p>($C = 1.3 \times 10^{-5}$ F to $C = 1.5 \times 10^{-5}$ F when rounded to 2 s.f.)</p> <p>Or</p> <ul style="list-style-type: none"> • $\frac{V_0}{2} = V_0 e^{-\frac{t_1}{RC}}$ (1) • $RC = t_{1/2} / \ln 2$ (1) • Records time for V to increase to $\frac{1}{2} V_0$ (3.4 s) (1) <p>(allow range 3.0 s to 3.5 s)</p> <ul style="list-style-type: none"> • $C = 1.5 \times 10^{-5}$ F, so choose 15 μF capacitor (1) <p>($C = 1.3 \times 10^{-5}$ F to $C = 1.5 \times 10^{-5}$ F when rounded to 2 s.f.) (1)</p> <p><u>Example of calculation</u></p> <p>V at time constant time = 0.63×6.00 V = 3.8 V</p> <p>Time from graph = 4.9 s</p> <p>$4.9 \text{ s} = C \times 3.3 \times 10^5 \Omega$</p> <p>$C = 1.48 \times 10^{-5}$ F</p>	<p>4</p>
----------------------------	---	-----------------

17 (b) (iv)	<ul style="list-style-type: none"> • Use of $Q = CV$ (ecf for C from (iii)) (1) • $Q = 9.0 \times 10^{-5} \text{ C}$ (1) <p><u>Example of calculation</u> $1.5 \times 10^{-5} \text{ F} \times 6.00 \text{ V} = 9.0 \times 10^{-5} \text{ C}$</p>	2
17 (b) (v)	<ul style="list-style-type: none"> • Use of $W = \frac{1}{2} CV^2$ (ecf for C from (iii)) • Or Use of $W = \frac{1}{2} QV$ (ecf for Q from (iv)) • Or Use of $W = \frac{1}{2} Q^2/C$ (ecf for C from (iii), for Q from (iv)) (1) • $W = 2.7 \times 10^{-4} \text{ J}$ (1) <p><u>Example of calculation:</u> $W = \frac{1}{2} \times 1.5 \times 10^{-5} \text{ F} \times (6.00 \text{ V})^2 = 2.7 \times 10^{-4} \text{ J}$</p>	2
	Total for question 17	16