

Question Number	Answer	Mark
<b>11(a)</b>	To limit the current (in the circuit) <b>Or</b> To avoid overheating/melting (in the circuit) (1)	<b>1</b>
<b>11(b)</b>	$\frac{I_W}{I_Z} = 1$ (1) as current is the same around a series circuit. (1) $\frac{v_W}{v_Z} = 0.25 \text{ (or 1:4)}$ (1) as the (cross-sectional) area / A is 4 times less for Z <b>Or</b> as the (cross-sectional) area / A is 4 times greater for W (1)  (for MP3, allow an answer “<1” ) (Do not award MP2 if value for MP1 is incorrect) (Do not award MP4 if value for MP3 is incorrect)	<b>4</b>
	<b>Total for question 11</b>	<b>5</b>