

| Question Number | Answer  | Mark      |
|-----------------|---|-----------|
| <b>17a</b>      | <p>Use of <math>V = W / Q</math> or <math>W = VIt</math> (1)</p> <p><math>\varepsilon = 1.56</math> (V) (1)</p> <p>Use of <math>V = IR</math> (1)</p> <p>Sum of e.m.f.s = Sum of p.d.s <b>Or</b> see <math>\varepsilon = V + Ir</math> (1)</p> <p><math>r = 2.6 \Omega</math> (1)</p> <p>(1)</p> <p><b>OR</b></p> <p>Use of <math>W = Pt</math></p> <p>With <math>P = I^2 R</math></p> <p>with <math>R = r + 12</math> (1)</p> <p>All other data correctly substituted (<math>50 = (0.107)^2 (r + 12) 300</math>) (1)</p> <p><math>r = 2.6 \Omega</math> (1)</p> <p>(1)</p> <p><u>Example of calculation</u> (1)</p> <p><math>\varepsilon = W / Q = (50 \text{ J}) / (0.107 \text{ A})(300 \text{ s}) = 1.56 \text{ V}</math></p> <p><math>\varepsilon = IR + Ir</math>, <math>1.56 \text{ V} = (0.107 \text{ A}) (12 \Omega) + (0.107 \text{ A}) r</math>,</p> <p><math>r = 2.56 \Omega</math></p> | <b>5</b>  |
| <b>17b</b>      | <p>(Increasing <math>R</math>) decreases <math>I</math></p> <p><b>Or</b> (Increasing <math>R</math>) gives <math>R</math> a greater share of the total resistance in the circuit (1)</p> <p>Less p.d. across internal resistance</p> <p><b>Or</b> <math>Ir</math> becomes less</p> <p>(Accept decrease in 'lost volts') (1)</p>   | <b>2</b>  |
| <b>17c</b>      | <p>Take readings for p.d. and current (1)</p> <p>Change resistance / <math>R</math> (1)</p> <p>Plot a graph of <math>V</math> against <math>I</math> (1)</p> <p>Gradient is <math>-r</math>. (1)</p> <p>(MP4 conditional on MP3)</p> <p>(Allow MP3/4 for graph of <math>I</math>-<math>V</math> with gradient <math>-1/r</math>)</p> <p>(A sketch graph of <math>V</math>-<math>I</math> with the gradient labelled <math>-r</math> can achieve MP3/4)</p>  | <b>4</b>  |
|                 | <b>Total for question 17</b>  | <b>11</b> |