

Question Number	Answer	Mark
13(a)	<p>Use of $R = \frac{\rho l}{A}$ (1)</p> <p>Use of cross-sectional area = width \times thickness (1)</p> <p>Thickness of layer of carbon = $1.2 \times 10^{-5} \text{ m}$ (1)</p> <p><u>Example of calculation</u></p> $8.8 \, \Omega = \frac{3.7 \times 10^{-5} \, \Omega \text{ m} \times 0.12 \text{ m}}{0.042 \text{ m} \times t}$ $t = 1.2 \times 10^{-5} \text{ m}$	3
13(b)(i)	<p>Use of $R = V/I$ to calculate I (1)</p> <p>Or ratio of resistances = ratio of p.d.s (1)</p> <p>Calculate p.d. across the internal resistance (see 0.1 V) (1)</p> <p>Or calculate whole circuit resistance (see 9.4 Ω) (1)</p> <p>$r = 0.63 \, \Omega$ (1)</p> <p><u>Example of calculation</u></p> $I = \frac{1.4}{8.8} = 0.16 \text{ A}$ $r = \frac{0.1 \text{ V}}{0.16 \text{ A}} = 0.63 \, \Omega$	3
13(b)(ii)	<p>Reading on voltmeter = 0.35 V (1)</p> <p><u>Example of calculation</u></p> $\frac{V}{1.4 \text{ V}} = \frac{3.0 \text{ cm}}{12.0 \text{ cm}}$ $V = 0.35 \text{ V}$	1
Total for question 13		7