

Question Number	Answer	Mark
17a	<p>Use of sum of e.m.f. = sum of p.d. (1)  Correct rearrangement leading to given equation (1)</p> <p><b>Or</b></p> <p>Total resistance of circuit = <math>R + r</math> (1)  Correct rearrangement with total resistance replaced by <math>\frac{\varepsilon}{I}</math> (1)</p> <p><u>Example of rearrangement</u>  <math>\varepsilon = I(R + r)</math>, so <math>\frac{\varepsilon}{I} = R + r</math>, so <math>R = \frac{\varepsilon}{I} - r</math></p>	2
17b	<p>Gradient calculation (to calculate <math>\varepsilon</math>) (1)  <math>\varepsilon = 1.5 \text{ V}</math> (1)  <math>r = 2 \Omega</math> (1)</p> <p><b>OR</b></p> <p><math>r = 2 \Omega</math> (read from y-intercept) (1)  Use of co-ordinates from the graph with the formula (1)  <math>\varepsilon = 1.5 \text{ V}</math> (1)</p>	3
17c	<p>Current (in <math>r/R</math>/circuit) decreases (1)  Reference to <math>P = I^2 r</math> (Do not allow if <math>R</math> used instead of <math>r</math>) (1)  <math>P</math> decreases, so student is correct (1)  (MP3 dependent on MP2)</p> <p><b>OR</b></p> <p><math>V</math> across <math>r</math> decreases (1)  Reference to <math>P = V^2/r</math> (Do not allow if <math>R</math> used instead of <math>r</math>) (1)  <math>P</math> decreases, so student is correct (1)  (MP3 dependent on MP2)</p> <p><b>OR</b></p> <p><math>V</math> across <math>r</math> decreases (1)  <math>P = VI</math> <b>and</b> current (in <math>r/R</math>/circuit) decreases (1)  <math>P</math> decreases, so student is correct (1)  (MP3 dependent on MP2)</p> <p><b>OR</b></p> <p>Current (in <math>r/R</math>/circuit) decreases (1)  <math>P = VI</math> <b>and</b> p.d. across <math>r</math> decreases (1)  <math>P</math> decreases, so student is correct (1)  (MP3 dependent on MP2)</p>	3