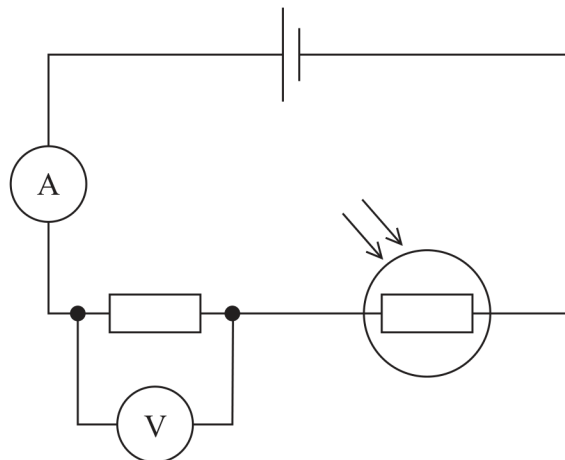


- 6 A light dependent resistor is connected in a circuit, as shown.



The intensity of light incident on the light dependent resistor decreases.

Which row of the table is correct?

	Ammeter reading	Voltmeter reading
<input type="checkbox"/> A	decreases	decreases
<input type="checkbox"/> B	increases	increases
<input type="checkbox"/> C	decreases	increases
<input type="checkbox"/> D	increases	decreases

(Total for Question 6 = 1 mark)