

Question number	Answer	Mark
3	<p>D</p> <p>The only correct answer is D because the charge stored on a capacitor = CV and all of the capacitors have the same p.d. of V, so doubling C doubles charge and having two capacitors doubles it again to $4Q$</p> <p>A is not the correct answer because it is not $4Q$ B is not the correct answer because it is not $4Q$ C is not the correct answer because it is not $4Q$</p>	(1)