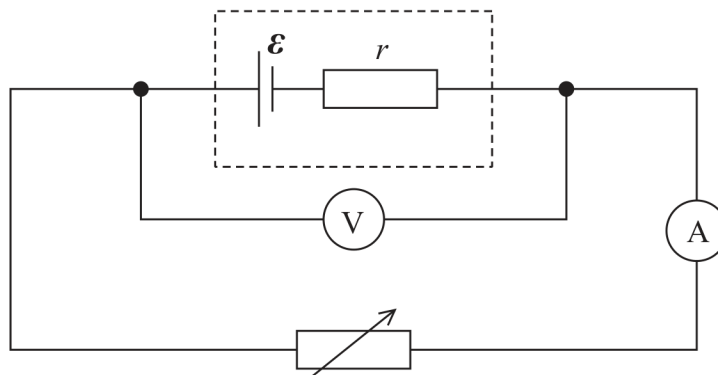


**Questions 5 and 6 refer to the following information.**

The diagram shows a circuit used to determine the internal resistance  $r$  and e.m.f.  $\mathcal{E}$  of a cell.



- 5 Corresponding values of potential difference  $V$  and current  $I$  were taken after adjusting the variable resistor. A graph of  $V$  on the  $y$ -axis against  $I$  on the  $x$ -axis was plotted.

Which of the following is correct?

- ☐ A The area underneath the graph is the total energy dissipated in the cell.
- ☐ B The gradient of the graph is  $r$ .
- ☐ C The graph shows that  $V$  and  $I$  are directly proportional.
- ☐ D The  $y$ -intercept of the graph is  $\mathcal{E}$ .

(Total for Question 5 = 1 mark)