

Question Number	Answer	Mark
19(a)	Power supply, ammeter, variable resistor and nichrome wire all in series (1)	2
	Voltmeter in parallel across nichrome wire (1)	
19(b)(i)	Gradient calculated Or value of p.d. read off for a corresponding length (1)	4
	Gradient uses more than half of the graph Or value of p.d. used is greater than 2.0V Or value of length used is greater than 0.5m (1)	
	Use of $R = \rho l / A$ and $R = V / I$ Or Use of $\rho = (\text{gradient} \times A) / I$ (1)	
	$\rho = 1.1 \times 10^{-6} \Omega \text{ m}$ (1)	
	(MP1 – Values read off graph need to be within ½ a square) (MP1 – Gradient should be in the range 4.1 – 4.2 Vm^{-1}) <u>Example of calculation</u> Gradient = $V / l = (4.15 \text{ V} / 1.00 \text{ m}) = 4.15 \text{ Vm}^{-1}$ $V / l = \rho l / A$, so $\rho = (\text{gradient} \times A) / I$ $= (4.15 \text{ Vm}^{-1} \times 5.31 \times 10^{-8} \text{ m}^2) / 0.200 \text{ A} = 1.10 \times 10^{-6} \Omega \text{ m}$	
19(b)(ii)	V value read from graph = 3.1V (1) Use of $P = VI$ (1) $P = 0.62 \text{ W}$ (1)	3
	(MP1 – allow use of resistivity equation with answer from (i) used to calculate V or R) (MP2 – allow combination of equations e.g. $R = V/I$ followed by $P = I^2 R$) (MP3 – allow variation of value if using resistivity value that rounds to $1.1 \times 10^{-6} \Omega \text{ m}$ from (i)) <u>Example of calculation</u> $P = VI = (3.1 \text{ V} \times 0.200 \text{ A}) = 0.62 \text{ W}$	
Total for Question 19		9