

2	<p>C is the correct answer as inverting $(1/Y + 1/Z)$ leads to $YZ / (Y + Z)$</p> <p>(1)</p> <p>A is not the correct answer as the section $(1/Y + 1/Z)$ has not been inverted)</p> <p>B is not the correct answer as this considers resistor X as a parallel resistor</p> <p>D is not the correct answer as this considers resistor X as a parallel resistor</p>
---	--