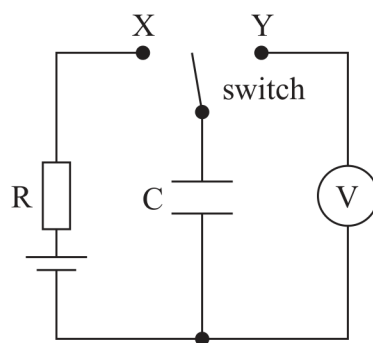


16 A student was investigating capacitors and set up the circuit shown.



The student planned to use the circuit to measure the potential difference V across the capacitor C as it was charged and discharged through the resistor R .

(a) Give two reasons why the circuit did not operate as intended.

(2)

.....

.....


.....

.....



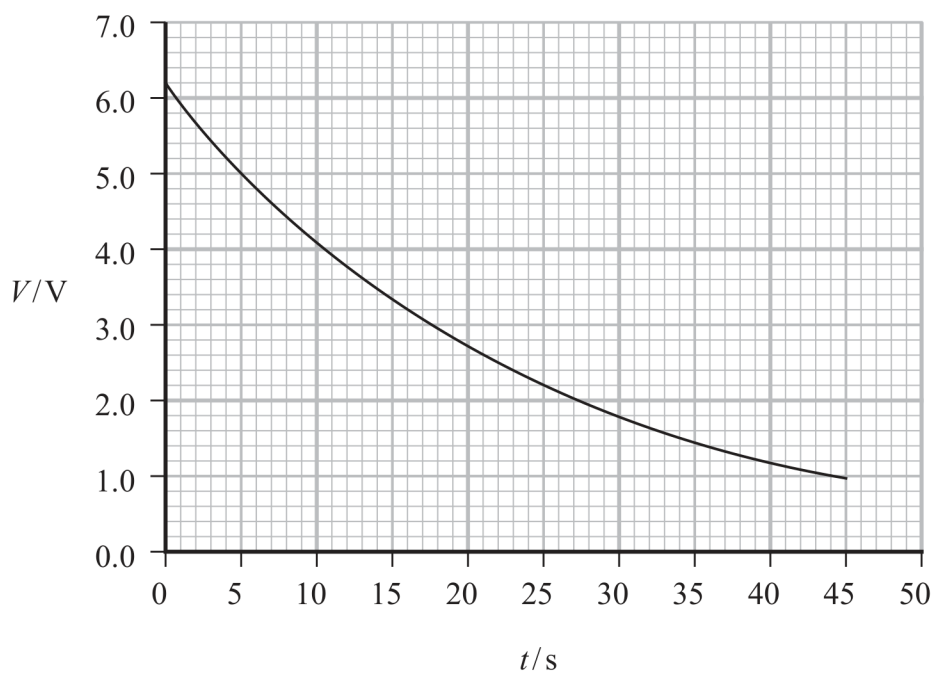(b) The student moved the switch from position X to position Y at time $t = 0$ s.

The student recorded values of V as t increased and plotted the graph shown.



The capacitance of capacitor C was $2.2\ \mu\text{F}$.

(i) Determine the resistance in the circuit when the switch was at position Y.

(3)

Resistance =



(ii) Determine the average current in the circuit between $t = 0\text{ s}$ and $t = 30\text{ s}$.

(4)

Average current =

(iii) Calculate the energy dissipated by the current in the circuit between $t = 0\text{ s}$ and $t = 30\text{ s}$.

(3)

Energy dissipated =

(Total for Question 16 = 12 marks)

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA