

9 A capacitor discharges through a resistor. The time constant of the circuit is 5 s.

What is the time taken, in s, for the charge on the plates of the capacitor to halve?

- ☐ A $0.5 \ln 2$
- ☐ B $0.5 \ln 5$
- ☐ C $2 \ln 5$
- ☐ D $5 \ln 2$

(Total for Question 9 = 1 mark)