

Question Number	Answer	Mark
12(a)	<p>Potential difference is the energy transfer per unit charge (1)(1)</p> <p>Energy is dissipated in the battery (1)</p> <p>Energy transferred to circuit is less than energy transferred in battery</p> <p><b>OR</b> (1)</p> <p>Potential difference is the energy transfer per unit charge (1)</p> <p>Voltage is dropped across the internal resistance (1)</p> <p>Less voltage is dropped across the rest of the circuit</p> <p>(MP3 via either method is conditional upon awarding MP2)</p> <p>(Allow “lost volts in the internal resistance” for MP2 via 2<sup>nd</sup> method)</p> <p>(Allow “terminal p.d. is lower” for MP3 via 2<sup>nd</sup> method)</p>	3
12(b)	<p>Use of <math>I = \frac{V}{R}</math> for the whole circuit (1)</p> <p>Use of <math>V = IR</math> for one of the resistors (1)</p> <p><math>V = 8.5 \text{ V}</math> (voltmeter reading) (1)</p> <p>(Award 1 mark for candidates using <math>V = IR</math> with any values given in the question)</p> <p><b>OR</b></p> <p>See ratio of p.d.s compared to ratio of resistances (1)</p> <p>With correct values substituted (1)</p> <p><math>V = 8.5 \text{ V}</math> (voltmeter reading) (1)</p> <p>(Award 1 mark for candidates using potential divider formula with any values given in the question).</p> <p><u>Example of calculation</u></p> $I = \frac{9.0 \text{ V}}{(270 + 15)\Omega} = 0.0316 \text{ A}$ $V = 0.0316 \text{ A} \times 270 \Omega = 8.53 \text{ V}$	3
12(c)	<p>Use of <math>V = \frac{W}{Q}</math> (1)</p> <p><math>W = 110 \text{ J}</math> (1)</p> <p>(Can award MP1 if candidate multiplies any value of V (of 9.0V or less) by the given charge)</p> <p><u>Example of calculation</u></p> $W = 9.0 \text{ V} \times 12 \text{ C} = 108 \text{ J}$	2
<b>Total for Question 12</b>		<b>8</b>