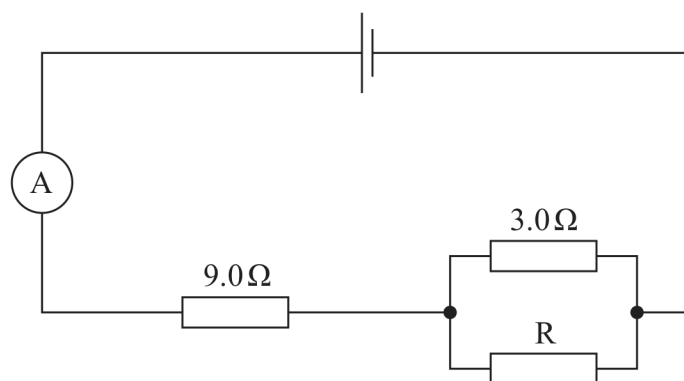


13 A student sets up the circuit shown with a cell of negligible internal resistance.

The ammeter displays a current of 0.14 A .



(a) Calculate a value for the resistance of the resistor R .

e.m.f. of the cell = 1.54 V

(4)

Resistance =

(b) The student made the $9.0\,\Omega$ resistor using a thin copper wire with a diameter of $0.15\,\text{mm}$.

(i) Show that the cross-sectional area of this wire was about $2 \times 10^{-8}\,\text{m}^2$.

(2)

(ii) Calculate the length of copper wire used by the student.

resistivity of copper = $1.68 \times 10^{-8}\,\Omega\text{m}$

(2)

Length of copper wire =

(iii) Calculate the drift velocity of the electrons in this copper wire.

number of charge carriers per unit volume = $8.49 \times 10^{28}\,\text{m}^{-3}$

current in copper wire = $0.14\,\text{A}$

(2)

Drift velocity =

(Total for Question 13 = 10 marks)