Question Number	Answer	Mark
13a U S S U A A A A A A A A A A A A A A A A	Use of $R = V/I$ (to find resistance of whole circuit) Subtracts 9Ω from 11Ω (to get 2Ω) Use of resistors in parallel formula $R = 6.0 \Omega$ (1) MP3 - Allow $2 = \frac{3R}{3+R}$) OR Use of $R = V/I$ (to find V across 9.0Ω resistor) Subtracts $1.26V$ from $1.54V$ (to get $0.28V$) Conservation of charge used to establish current in R ($0.467 A$) $R = 6.0 \Omega$ Example of calculation $R = V/I$ for whole circuit $= 1.54 V / 0.14 A = 11 \Omega$ Resistance of parallel section $= 11 \Omega - 9 \Omega = 2 \Omega$ $\frac{1}{RP} = \frac{1}{R_1} + \frac{1}{R_2}$, so $\frac{1}{R} = \frac{1}{2} - \frac{1}{3} = \frac{1}{6}$ So $R = 6 \Omega$ OR $V = IR$ for 9.0Ω resistor $= 0.14 A \times 9.0 \Omega = 1.26 V$ and across 3.0Ω resistor and resistor $R = 1.54 V - 1.26 V = 0.28 V$ For 3.0Ω resistor) $I = V/R = 0.28 V / 3.0 \Omega = 0.0933 A$ Current in resistor $R = 0.14 A - 0.0933 A = 0.0467 A$ $R = V/I = 0.28 V / 0.0467 A = 6.0 \Omega$	4

13bi	Use of cross-sectional area = πr^2	(1)	
	Cross-sectional area = $1.8 \times 10^{-8} \text{ (m}^2\text{)}$	(1)	2
	("Show that" so units not required)		
	(MP1 – not awarded if diameter is used)		
	Example of calculation		
	$\frac{2 \times 4 \times 10^{-3} \text{ m}}{2 \times 10^{-3} \text{ m}} = \frac{2}{2} = \frac{0.15 \times 10^{-3} \text{ m}}{2} = \frac{1.77 \times 10^{-8} \text{ m}^2}{2}$		
	cross-sectional area = $\pi r^2 = \pi \left(\frac{0.15 \times 10^{-3} \text{ m}}{2}\right)^2 = 1.77 \times 10^{-8} \text{ m}^2$		
13bii	Use of $R = \rho I/A$	(1)	
10011	Length of copper wire = 9.5 m	(1)	2
		(-)	_
	(e.c.f. from (b)(i))		
	(Answer using "show that" value = 10.7 m)		
	Enemals of calculation		
	Example of calculation $RA = (9.0.0)(1.77 \times 10^{-8} m^2)$		
	$l = \frac{RA}{\rho} = \frac{(9.0 \Omega)(1.77 \times 10^{-8} \text{m}^2)}{(1.68 \times 10^{-8} \text{\Omega m})} = 9.48 \text{ m}$		
13biii	Use of $I = nqvA$	(1)	
	$v = 5.8 \times 10^{-4} \text{ m s}^{-1}$	(1)	2
	(e.c.f. from b(i))		
	(Answer using "show that" value = $5.2 \times 10^{-4} \text{ m s}^{-1}$) (ignore minus sign on answer)		
	(ignore ininus sign on answer)		
	Example of calculation		
	$v = \frac{1}{nqA} = \frac{(0.14 \text{ A})}{(8.49 \times 10^{28} m^{-3})(1.60 \times 10^{-19} C)(1.77 \times 10^{-8} m^2)} = 5.8 \times 10^{-4} \text{ m s}^{-1}$		
	$nqA = (8.49 \times 10^{28} m^{-3})(1.60 \times 10^{-19} C)(1.77 \times 10^{-8} m^2) = 3.6 \times 10^{-11} M S$		

10

Total for question 13