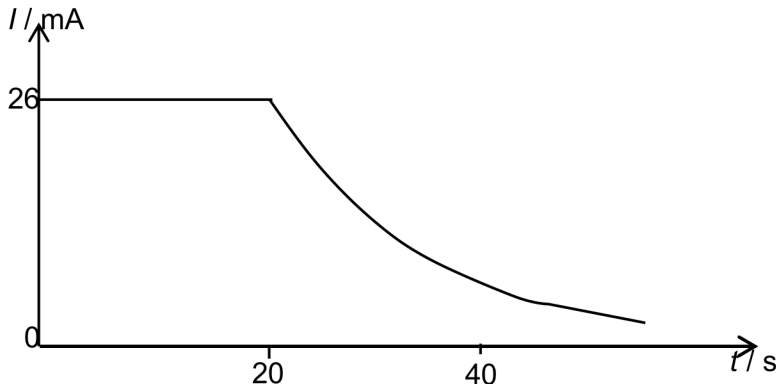


Question Number	Answer	Mark
14a	<p>The capacitor stores charge/energy (1)</p> <p>(if the switch is open) the capacitor discharges through resistor/controller</p> <p>Or</p> <p>(if the switch is open) the p.d across the resistor/controller is maintained by the capacitor (1)</p> <p>p.d. across capacitor will remain high enough to operate the controller for a short time</p> <p>Or</p> <p>current in circuit will remain high enough to operate the controller for a short time</p> <p>Or</p> <p>charge/energy stored is limited and will only last for a short time (1)</p>	3
14b	<p>Use of $\ln V = \ln V_0 - \frac{t}{RC}$ (1)</p> <p>$t = 24 \text{ s}$ (1)</p> <p><u>Example of calculation</u></p> $\ln 4 = \ln 12 - \frac{t}{470 \times 47 \times 10^{-3} \text{ s}}$ <p>$t = 24.3 \text{ s}$</p>	2
14c	<p>Horizontal line of non-zero I from 0 to 20 s (1)</p> <p>(Initial value of) $I = 26 \text{ mA}$ (1)</p> <p>(From 20 s) approximate exponential decrease (1)</p> <p>Approximately drops to 1/3 after about 44 s (24 s after start of decrease) (1)</p> <p>ECF depending on calculation from (b)</p> <p><u>Example of calculation</u></p> $I = 12 \text{ V} / 470 \Omega = 0.026 \text{ A}$ 	4
Total for question 14		9