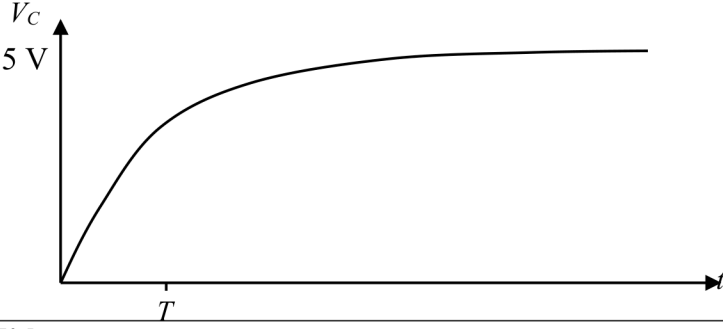


Question Number	Answer	Mark
<b>15ai</b>	<p>exponential growth curve starting at origin and levelling at 5 V (accept <math>V_0</math>) (1)</p> <p>levelling off after at approx. 4 to 5 time constants  <b>Or</b> curve through approx 2/3 of maximum at <math>T</math> (accept labelled as 3.2 V or 63%) (1)</p> <p><u>Example of graph</u></p> 	<b>2</b>
<b>15aii</b>	<p><b>Either</b> (1)</p> <p>p.d. would decrease exponentially from 5 V  Or p.d. would decrease exponentially to 0 V</p> <p>Because the sum of the p.ds across the capacitor and resistor must always add up to the supply p.d. (1)</p> <p><b>Or</b>  as capacitor charges then p.d. across resistor must decrease from 5 V. (1)</p> <p>so current in resistor decreases so rate of change of p.d. decreases (1)</p>	<b>2</b>
<b>15aiii</b>	<p><math>5 = V_R + V_C</math> (1)</p> <p>Use of <math>V_R = V_0 e^{-t/RC}</math> and <math>V_0 = 5</math> to give required equation (1)</p>	<b>2</b>
<b>15b</b>	<p>Use of <math>V_C = 5 - 5e^{-t/RC}</math> (1)</p> <p>Takes <math>\ln</math> of both sides of equation (1)</p> <p><math>C = 48 \mu\text{F}</math> so select <math>47 \mu\text{F}</math> (1)</p> <p><u>Example of calculation</u></p> <p><math>3.3 = 5 - 5e^{-3.5/68000 \times C}</math></p> <p><math>\ln \frac{1.7}{5} = - \frac{3.5}{68000 \times C}</math></p> <p><math>1.08 C = 5.15 \times 10^{-5}</math></p> <p><math>C = 4.77 \times 10^{-5} \text{ F}</math></p> <p>So <math>47 \mu\text{F}</math></p>	<b>3</b>
<b>Total for question 15</b>		<b>9</b>