

9	D is the correct answer because $Q = Q_o e^{-\frac{t}{RC}}$ and $RC = 5 \text{ s}$	1
---	--	---