

4	<p>A is the correct answer</p> <p>B is not the correct answer as there is a larger proportion of the total pd across the LDR</p> <p>C is not the correct answer as current in the circuit decreases</p> <p>D is not the correct answer as current in the circuit decreases and there is a larger proportion of the total pd across the LDR</p>	(1)
5		(1)