

Question Number	Answer	Mark
12a	Ammeter in series with cell and an external component with resistance (1) Voltmeter parallel with cell (1) Variable resistor included in circuit (1)	3
12b	(Uses conservation of energy to) obtain the equation $\varepsilon = V + Ir$ (1) Compares $\varepsilon = V + Ir$ with $y = mx + c$ (1) e.m.f. is the y-intercept of the graph (1) Internal resistance is the negative of the gradient (1)	4
	Total for question 12	7