2	C is the correct answer	(1)	
	A is not the correct answer as there is a small current In the reverse direction		
	correct answer as there is a small current In the reverse direction		
	D is not the correct answer as there is a small current when the p.d. $< 0.7 \text{ V}$		