

- 9 Two copper wires are placed in series in a complete circuit. The electrons in the two wires have different values of drift velocity.

Which of the following must be different for the two wires?

- ☐ A charge carrier density
- ☐ B cross-sectional area
- ☐ C current
- ☐ D length

(Total for Question 9 = 1 mark)