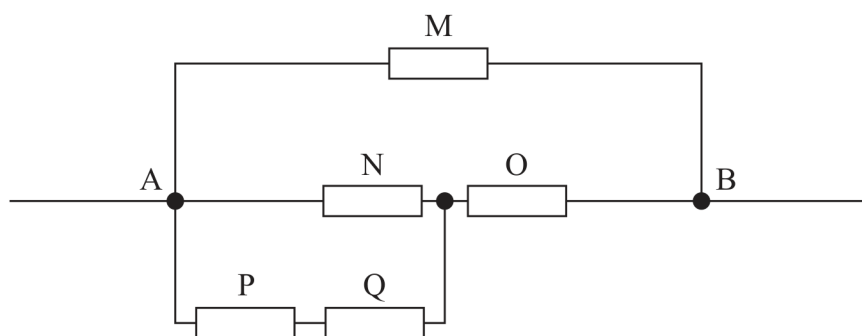


- 15 (a) Two resistors of resistance  $R_1$  and  $R_2$  are connected in parallel in a circuit.

Derive a formula for the total resistance  $R_T$  of the combination.

(3)

- (b) The diagram shows a combination of five resistors, M, N, O, P and Q. Each resistor has a resistance of  $5.0\ \Omega$ .



- (i) Show that the resistance between points A and B is about  $3\ \Omega$ .

(3)

- (ii) A student is told to modify the combination of resistors so that the combined resistance between A and B is greater than  $5.0\ \Omega$ . She cannot change the arrangement of the resistors, but she can replace one of the  $5.0\ \Omega$  resistors with a  $20.0\ \Omega$  resistor.

Explain, without further calculations, which of the five resistors should be replaced.

(2)

(Total for Question 15 = 8 marks)