

Question Number	Answer	Mark
<b>14a</b>	Use of $I = V / R$ (1)	<b>2</b>
	$I = 0.15 \text{ mA}$ which is consistent (with the value on the graph) (1)	
	<u>Example of calculation</u>	
	$I = 5.0 \text{ V} / 33 \text{ k}\Omega = 1.5 \times 10^{-4} \text{ A} = 0.15 \text{ mA}$	
<b>14b</b>	The current would vary with time in the same way as on ammeter $A_1$ (1)	<b>2</b>
	Because (current is same everywhere) in a series circuit (1)	
<b>14c</b>	<b>Either</b>	<b>3</b>
	Takes two corresponding values of $I$ and $t$ from graph (1)	
	Use of $\ln I = \ln I_0 - t/RC$ (1)	
	$C = 2.27 \times 10^{-4} \text{ F}$ ( $2.0 \times 10^{-4} \text{ F}$ - $2.3 \times 10^{-4} \text{ F}$ ) (1)	
	<b>Or</b>	
	Draws initial tangent to curve and determines $t$ intercept: $T$ (1)	
	(0.65-0.75 s) (1)	
	Use of $T = RC$ (1)	
	$C = 2.2 \times 10^{-4} \text{ F}$ ( $2.0 \times 10^{-4} \text{ F}$ - $2.3 \times 10^{-4} \text{ F}$ ) (1)	
	<b>Or</b>	
	Read value of $t$ at which $I = I_0 / e$ (0.56 A, 0.7 s) (1)	
	Use of $T = RC$ (1)	
	$C = 2.1 \times 10^{-4} \text{ F}$ ( $2.0 \times 10^{-4} \text{ F}$ - $2.3 \times 10^{-4} \text{ F}$ ) (1)	
	<u>Example of calculation</u>	
	eg $I = 0.04 \text{ mA}$ and $t = 10 \text{ s}$	
	$\ln 0.04 = \ln 0.152 - \frac{10\text{s}}{C \times 33\text{k}}$	
	$C = 2.27 \times 10^{-4} \text{ F}$ range: $2.0 \times 10^{-4} \text{ F}$ - $2.3 \times 10^{-4} \text{ F}$	
<b>14d</b>	Attempt to determine an area under the curve (1)	<b>2</b>
	$Q = 1.1 \times 10^{-3} \text{ C}$ ( $1.0 \times 10^{-3} \text{ C}$ to $1.2 \times 10^{-3} \text{ C}$ ) (1)	
	<b>Or</b>	
	Use of $Q = CV$ with 5.0 V (1)	
<b>14e</b>	$Q = 1.1 \times 10^{-3} \text{ C}$ (allow ecf from (c)) (1)	<b>2</b>
	Use of $W = \frac{QV}{2}$ or $W = \frac{1}{2} CV^2$ or $W = Q^2/2C$ (1)	
	$W = 2.8 \times 10^{-3} \text{ J}$ (allow ecf from 14c and 14d) (1)	
	<u>Example of calculation</u>	
	$W = 1.1 \times 10^{-3} \text{ C} \times 5 \text{ V} / 2 = 2.8 \times 10^{-3} \text{ J}$	
<b>Total for question 14</b>		<b>11</b>