

Question Number	Answer	Mark
<b>14(a)</b>	<p>Uses <math>R = V/I</math> for resistor (1)</p> <p><b>Or</b> uses potential divider</p> <p>Uses <math>R = V/I</math> for thermistor (1)</p> <p><math>R</math> for thermistor = <math>19\ \Omega</math> (1)</p> <p>Temperature = <math>32 - 36^\circ\text{C}</math> (1)</p> <p><u>Example of calculation</u></p> <p><math>R = V/I</math>, <math>I = V/R</math> (for resistor), <math>I = (3.42\ \text{V}) / (11.5\ \Omega) = 0.297\ \text{A}</math></p> <p><math>R = V/I</math> (for thermistor) = <math>(9.00 - 3.42\ \text{V}) / (0.297\ \text{A}) = 18.8\ \Omega</math></p>	<b>4</b>
<b>14(b)</b>	<p>Increased e.m.f. leads to greater current (1)</p> <p>(Increased current leads to) greater temperature (1)</p> <p>Resistance of thermistor would decrease (1)</p> <p>(The proportion of the total p.d. across thermistor would decrease so) voltmeter reading would more than double so student incorrect (1)</p> <p>(For MP4 there needs to be a clear conclusion that the student is incorrect)</p>	<b>4</b>
	<b>Total for question 14</b>	<b>8</b>