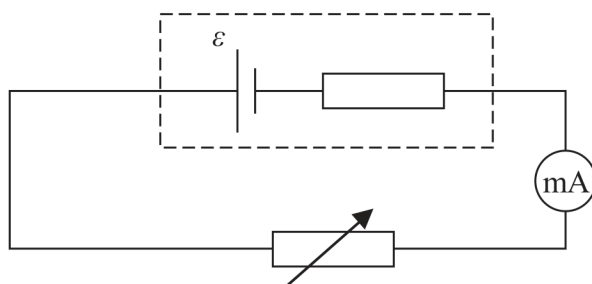


- 17 A cell of e.m.f. ε is connected in series with a variable resistor with resistance R as shown. The internal resistance of the cell is r .



When R is $12\ \Omega$, the reading on the ammeter is 107 mA . The circuit is switched on for 300 seconds. In this time, 50 J of energy is transferred by the cell.

- (a) Calculate r .

(5)


$r = \dots\dots\dots$

(b) Increasing R would make the terminal potential difference value closer to ε .

Explain why, without further calculation.

(2)

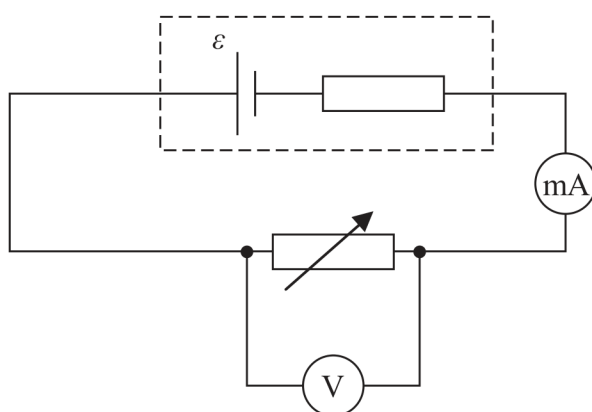(c) A voltmeter is added to the circuit as shown.



Explain how this circuit can be used to determine a value for r using a graphical method.

(4)