

Question Number	Answer	Mark
17a	<p>Either</p> <p>Uses resistors in parallel formula correctly (1)</p> <p>Adds series resistance (1)</p> <p>Use of $V = IR$ to find whole circuit current (1)</p> <p>Current in the $6.0\ \Omega$ resistor = 0.67A (1)</p> <p>Use of $Q = It$ (1)</p> <p>4.2×10^{18} (electrons) (1)</p> <p>Or</p> <p>Uses resistors in parallel formula correctly (1)</p> <p>Uses potential divider to calculate V across parallel section (1)</p> <p>Use of $V = IR$ to find current in $6.0\ \Omega$ resistor (1)</p> <p>Current in the $6.0\ \Omega$ resistor = 0.67A (1)</p> <p>Use of $Q = It$ (1)</p> <p>4.2×10^{18} (electrons) (1)</p> <p><u>Example of calculation</u></p> <p>$\frac{1}{R_p} = \frac{1}{3.0\ \Omega} + \frac{1}{6.0\ \Omega}$, so $R_{\text{parallel}} = 2.0\ \Omega$</p> <p>Total circuit resistance = $4.0\ \Omega + 2.0\ \Omega = 6.0\ \Omega$</p> <p>$I = V / R = 12\ \text{V} / 6.0\ \Omega = 2.0\ \text{A}$</p> <p>Current in $6.0\ \Omega$ resistor is $1/3$ of $2.0\text{A} = 0.67\ \text{A}$</p> <p>No. of electrons per second = $\frac{\text{current}}{\text{charge per electron}} = \frac{0.67\ \text{A}}{1.60 \times 10^{-19}\text{C}}$</p> <p>= 4.2×10^{18} electrons per second</p>	6
17b	<p>(Student is correct that) resistance in circuit/parallel is greater (1)</p> <p>V is the same (1)</p> <p>So if student uses $P = V^2/R$ (1)</p> <p>Power in whole circuit would be less, so student incorrect (1)</p> <p>Or</p> <p>(Student is correct that) resistance in circuit/parallel is greater (1)</p> <p>This leads to current being lower (1)</p> <p>So if student used $P = VI$ with same V (1)</p> <p>Power in whole circuit would be less, so student incorrect (1)</p> <p>Or</p> <p>(Student is correct that) resistance in circuit/parallel is greater (1)</p> <p>This leads to current being lower (1)</p> <p>Effect of decreasing current > the effect of increasing resistance (1)</p> <p>Power in whole circuit would be less, so student incorrect (1)</p> <p>(MP4 via any method is dependent on awarding MP2 & MP3)</p>	4
Total for question 17		10