

Question Number	Answer	Mark																																								
*14	<p>This question assesses a student’s ability to show a coherent and logically structured answer with linkages and fully-sustained reasoning. Marks are awarded for indicative content and for how the answer is structured and shows lines of reasoning. The following table shows how the marks should be awarded for indicative content.</p> <table><tr><th>IC points</th><th>IC mark</th><th>Max linkage mark</th><th>Max final mark</th></tr><tr><td>6</td><td>4</td><td>2</td><td>6</td></tr><tr><td>5</td><td>3</td><td>2</td><td>5</td></tr><tr><td>4</td><td>3</td><td>1</td><td>4</td></tr><tr><td>3</td><td>2</td><td>1</td><td>3</td></tr><tr><td>2</td><td>2</td><td>0</td><td>2</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr></table> <p>The following table shows how the marks should be awarded for structure and lines of reasoning.</p> <table><tr><td></td><td>Number of marks awarded for structure of answer and sustained line of reasoning</td></tr><tr><td>Answer shows a coherent and logical structure with linkages and fully sustained lines of reasoning demonstrated throughout</td><td>2</td></tr><tr><td>Answer is partially structured with some linkages and lines of reasoning</td><td>1</td></tr><tr><td>Answer has no linkages between points and is unstructured</td><td>0</td></tr></table> <p>Indicative content</p> <ul style="list-style-type: none">Resistance of LDR decreasesDue to increase in number of (conduction) electronsSo the resistance of circuit decreasesOr This results in greater current in circuit/LDR/resistore.m.f. of the circuit is the sameAnd due to $P = VI$ Or $P = I^2R$ Or $P = V^2/R$ (for whole circuit)The power dissipated by the circuit increases <p>(IC2 – allow “number of charge carriers” or “charge carrier density”) (IC4 – allow “total circuit voltage/p.d.” for “e.m.f.”) (IC6 – needs to be related to correct V,I,R for whole circuit)</p>	IC points	IC mark	Max linkage mark	Max final mark	6	4	2	6	5	3	2	5	4	3	1	4	3	2	1	3	2	2	0	2	1	1	0	1	0	0	0	0		Number of marks awarded for structure of answer and sustained line of reasoning	Answer shows a coherent and logical structure with linkages and fully sustained lines of reasoning demonstrated throughout	2	Answer is partially structured with some linkages and lines of reasoning	1	Answer has no linkages between points and is unstructured	0	6
IC points	IC mark	Max linkage mark	Max final mark																																							
6	4	2	6																																							
5	3	2	5																																							
4	3	1	4																																							
3	2	1	3																																							
2	2	0	2																																							
1	1	0	1																																							
0	0	0	0																																							
	Number of marks awarded for structure of answer and sustained line of reasoning																																									
Answer shows a coherent and logical structure with linkages and fully sustained lines of reasoning demonstrated throughout	2																																									
Answer is partially structured with some linkages and lines of reasoning	1																																									
Answer has no linkages between points and is unstructured	0																																									
Total for question 14		6																																								