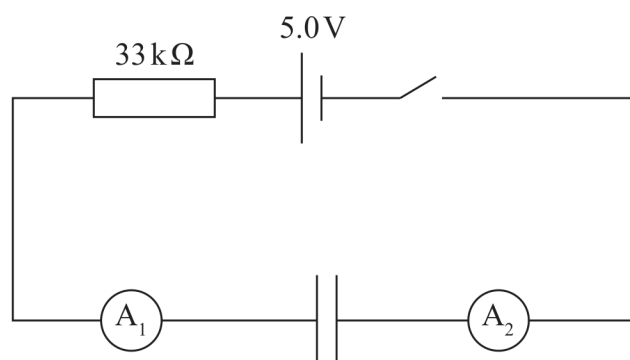
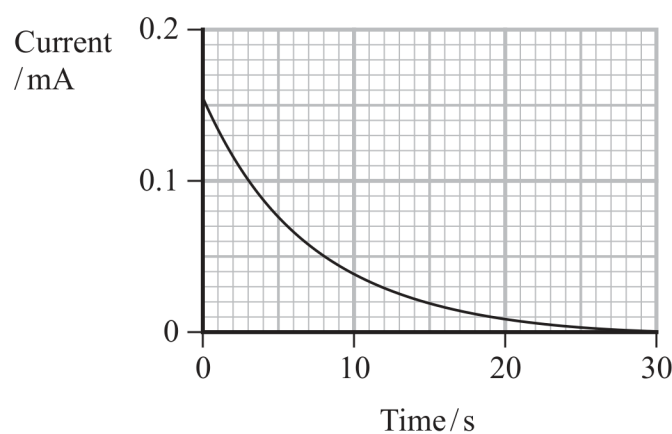


14 A student built the circuit shown. The capacitor was initially uncharged.



She closed the switch and plotted a graph of current on ammeter A₁ against time.



- (a) Determine whether the initial value of current on the graph is consistent with the values stated on the circuit diagram.

(2)

- (b) Explain how the current on ammeter A₂ would vary over the same time interval.

(2)

(c) Determine the capacitance of the capacitor.

(3)

.....

.....

.....

.....

.....

Capacitance =

(d) Determine the charge stored on the capacitor after 30 s.

(2)

.....

.....

.....

.....

Charge stored on capacitor after 30 s =

(e) Determine the maximum energy stored by the capacitor.

(2)

.....

.....

.....

.....

Maximum energy =

(Total for Question 14 = 11 marks)