

Question Number	Answer	Mark
14(a)	10°C corresponds to 2.0 Ω (1)	6
	Use of ratio of resistances (1)	
	Use of corresponding ratio of p.d.s (1)	
	To a p.d. of 0.7(06) V (1)	
	If temperature goes below this level then resistance of thermistor increases (1)	
	So p.d. to heater (switch) increases and so heater switch does perform as required (1)	
	<u>Example of calculation</u>	
	$\frac{V}{6.0} = \frac{2.0}{15 + 2.0}$	
	$V = 0.706 \text{ V}$	
	Or	
	10°C corresponds to 2.0 Ω (1)	
	Use of $I = V/R$ for whole circuit (1)	
	Use of $V = IR$ for thermistor (1)	
	To a p.d. of 0.7(06) V (1)	
14(b)	If temperature goes below this level then resistance of thermistor increases (1)	2
	So p.d. to heater (switch) increases and so heater switch does perform as required (1)	
	<u>Example of calculation</u>	
	$I = 6.0 \text{ V} / (2 + 15) \Omega$ $= 0.353 \text{ A}$ $V = 0.353 \text{ A} \times 2.0 \Omega$ $= 0.706 \text{ V}$	
14(b)	Increase in temperature results in more electrons released (1)	2
	Or Increase in temperature results in more electrons moving into conduction band (1)	
	So resistance decreases (dependent on MP1) (1)	
	[allow converse argument]	
Total for question 14		8