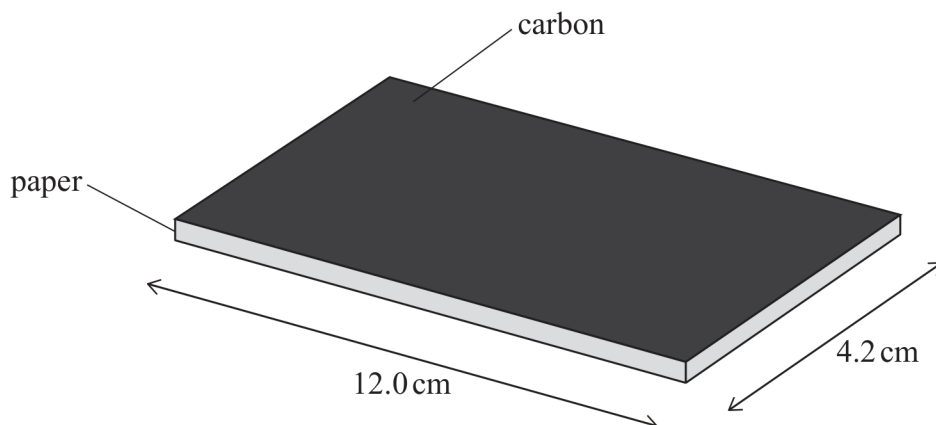


13 'Resistivity paper' is paper covered with a thin layer of carbon.

The distance between the ends of a piece of resistivity paper is 12.0 cm. The resistivity paper is 4.2 cm wide as shown.



The resistance between the ends of the resistivity paper is 8.8Ω .


(a) Calculate the thickness of the layer of carbon.

resistivity of carbon = $3.7 \times 10^{-5} \Omega \text{m}$

(3)

Thickness of layer of carbon =

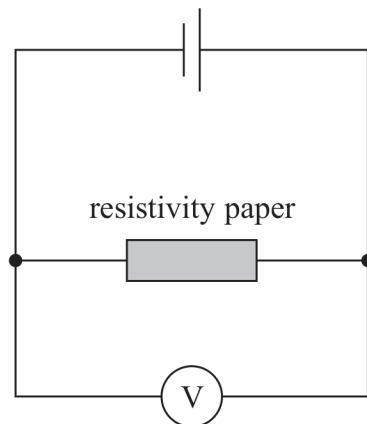- (b) A student connected the ends of the resistivity paper to a cell of e.m.f. 1.5 V and a voltmeter, as shown.



- (i) The reading on the voltmeter was 1.4 V .

Calculate the internal resistance of the cell.

(3)

Internal resistance =

- (ii) The connection to the right-hand terminal of the voltmeter was moved to a distance of 3.0 cm from the left-hand side of the resistivity paper.

Determine the reading on the voltmeter.

(1)

Reading on voltmeter =

(Total for Question 13 = 7 marks)