

3	<p><b>D is the correct answer</b></p> <p>A is not the correct answer as increasing temperature causes an increase in current for this circuit.</p> <p>B is not the correct answer as increasing temperature causes an increase in current for this circuit.</p> <p>C is not the correct answer as increasing temperature decreases the p.d. across the thermistor, but increases the p.d. across the fixed resistor.</p>	(1)
---	--	-----