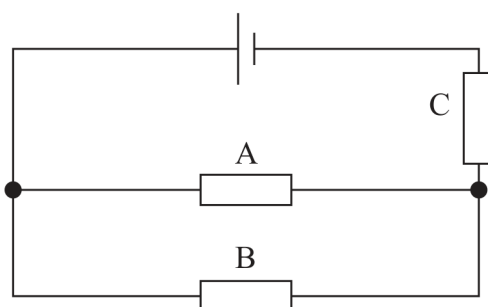


- 15 The diagram shows a circuit containing three identical resistors, A, B and C. The cell has negligible internal resistance.



- *(a) Explain how measurements of current and potential difference could be used to demonstrate that charge and energy are both conserved in this circuit. Your answer should refer to resistors A, B and C.

(6)


- (b) (i) Calculate the total resistance of the circuit.

resistance of each resistor = $12.5 \, \Omega$

(3)

Total resistance =

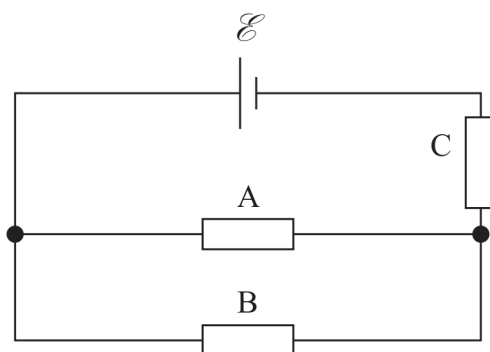- (ii) The resistors are connected to a different cell, with e.m.f. \mathcal{E} , as shown. The cell has an internal resistance.



Describe how a single ammeter reading can be used to determine the internal resistance of the cell. You should add to the diagram to show the position of this ammeter.

(3)