

7	<p>A is the correct answer (Reading on V_1 decreases, readings on V_2 and A increase)</p> <p>B is not the correct answer as the decreased resistance of the thermistor will lead to a greater share of the p.d. across the fixed resistor</p> <p>C is not the correct answer as the meter readings show what would happen if the temperature decreased</p> <p>D is not the correct answer as none of the three meter readings would change in the ways stated</p>	(1)
---	--	-----