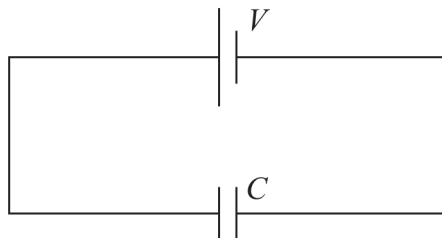
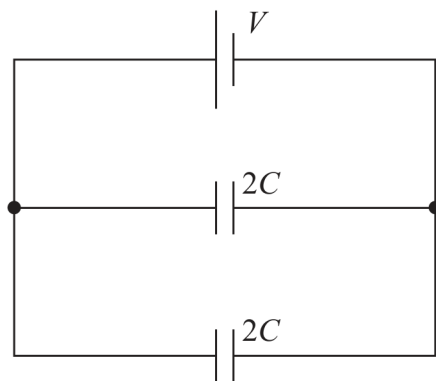


- 3 A potential difference (p.d.) V is connected across a capacitor of capacitance C .
The charge stored on the capacitor is Q .



The capacitor is replaced with two capacitors, each of capacitance $2C$, in parallel.



What is the total charge stored?

- ☐ A $\frac{Q}{4}$
- ☐ B Q
- ☐ C $2Q$
- ☐ D $4Q$